

Sequential Circuits

Representation of a sequential circuit?

State graph

$$G = (X, Y, S, T, O)$$

define the transition function: mk

 m_k = sum of the Boolean function of the transitions that have as target a state where m_k =1



Pirouz Bazargan Sabet

Digital Design

February 2010

Sequential Circuits

Representation of a sequential circuit?

State graph

$$G = (X, Y, S, T, O)$$

define the *output function* : y_i

 $y_i = \text{sum of the output conditions concerning } y_i$




Pirouz Bazargan Sabe

gital Design

February 2010

Sequential Circuits

Example

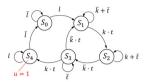

$$M_0 = M_0 \cdot \bar{l} + M_4 \cdot \bar{l}$$

$$M_1 = M_0 \cdot l + M_1 \cdot (\bar{k} + \bar{t}) + M_3 \cdot \bar{k}t$$

$$M_2 = M_2 \cdot (k + \bar{t}) + M_1 \cdot kt$$

$$M_3 = M_3 \cdot \bar{t} + M_2 \cdot \bar{k}t$$

$$M_4 = M_4 \cdot l + M_3 \cdot kt$$




irouz Bazargan Sabet

Digital Design

February 2010

Sequential Circuits

Example

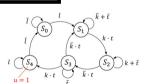

$$M_0 = M_0 \cdot \bar{l} + M_4 \cdot \bar{l}$$

$$M_1 = M_0 \cdot l + M_1 \cdot (\bar{k} + \bar{t}) + M_3 \cdot \bar{k}t$$

$$M_2 = M_2 \cdot (k + \bar{t}) + M_1 \cdot kt$$

$$M_3 = M_3 \cdot \bar{t} + M_2 \cdot \bar{k}t$$

$$M_4 = M_4 \cdot l + M_3 \cdot kt$$

$$u = M_{\Delta}$$



Pirouz Bazargan Sabet

 $Digital\ Design$

February 2010