

$$G = (X, Y, S, T, O)$$

O: output set conditions

$$o \in O$$
,  $o = (y, s, c)$ 

 $y \in Y$ : output variable

 $s \in S$  : state

 $c \in B_n$ : output set condition



Pirouz Bazargan Sabet

Digital Design

February 2010

## **Sequential Circuits**

Representation of a sequential circuit?

State graph

Transpose into a graphic representation the expected behavior of a sequential system

$$G = (X, Y, S, T, O)$$



Pirouz Bazargan Sabe


Digital Design

February 2010

### Sequential Circuits

 $\bigcirc$  Let consider a graph G = (X, Y, S, T, O)

Graphic representation of **G** 

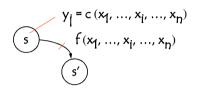



irouz Bazargan Sabet

Digital Design

February 2010

## **Sequential Circuits**

#### Example

Two signals **a**, **b** each transmitting a series of bits (1 bit at a cycle)


Design a system that sets a flag d if the value transmitted by a is different than b






Pirouz Bazargan Sabet

nguai Design

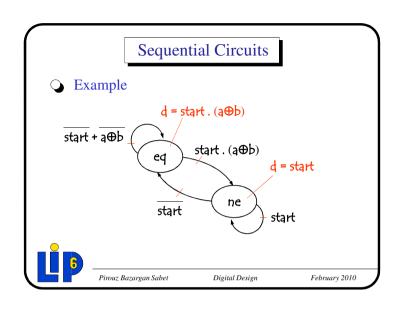

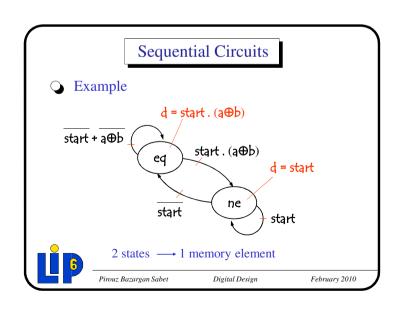

Representation of a sequential circuit?

State graph

G = (X, Y, S, T, O)

define the number of memory elements required to represent S: M



Pirouz Bazargan Sabet

Digital Design

February 2010

#### **Sequential Circuits**

Representation of a sequential circuit?

State graph

$$G = (X, Y, S, T, O)$$


define the number of memory elements required to represent S:M


represent each state s by a vector of M



Pirouz Bazargan Sabet

nguai Design

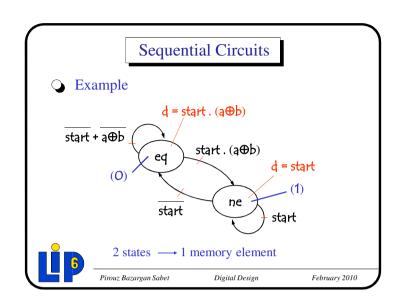

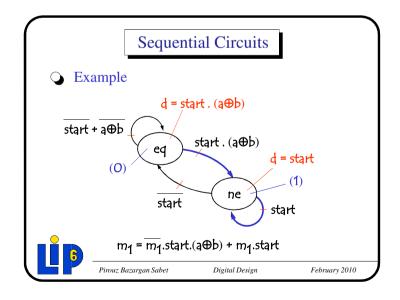

Representation of a sequential circuit?

State graph

$$G = (X, Y, S, T, O)$$

define the transition function :  $m_k$ 

 $m_k$  = sum of the Boolean function of the transitions that have as target a state where  $m_k$ =1



Pirouz Bazargan Sabet

Digital Design

February 2010

## **Sequential Circuits**

Representation of a sequential circuit?

State graph

$$G = (X, Y, S, T, O)$$


define the *output function* :  $y_i$ 


 $y_i = \text{sum of the output conditions concerning } y_i$ 




Pirouz Bazargan Sabe


nguai Design

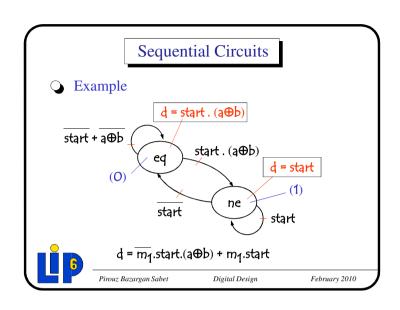

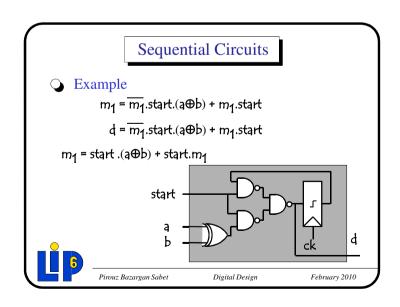

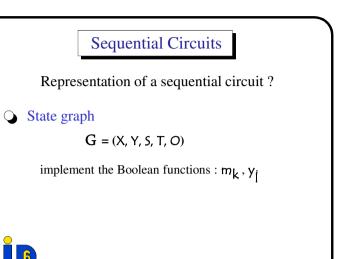

Digital Design

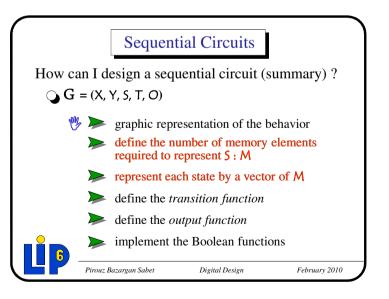

How can I design a sequential circuit (summary)?

$$\bigcirc$$
 G = (X, Y, S, T, O)

> check the completeness

for each state s:

$$\sum_{i(s,s'_i,f_i)} f_i = 1$$

check the exclusivity

for each state s:

$$\sum_{\substack{=(s,s'_{i},f_{i})\\=(s,s'_{j},f_{j})\\i\neq j}} f_{i} \cdot f_{j} = 0$$



Pirouz Bazargan Sabet

Digital Design